 


# Lab 3: Light Sensor

*Liam Snow*



Professor Schaumont

ECE 3829 Advanced Digital System Design With FPGAs

WORCESTER POLYTECHNIC INSTITUTE


February 2024

# Introduction

The goal of this lab was to create an SPI interface to interact with the `ADC081S021` light sensor over the Basys 3's PMOD extension port and display the reading on the seven segment display. I separated out the task into multiple modules to create a more organized approach. I created one module that would handle everything for the light sensor, including the SPI protocol and creating a slower clock for the interface. Then, I created a module to handle displaying numbers on the seven segment display. Finally, I created a module to convert the master  $100MHz$  clock to a slower  $10MHz$  clock.

# Solution

## Diagram

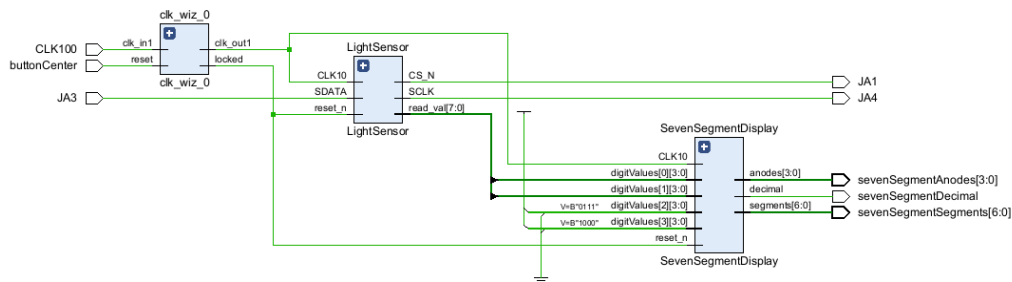

## Clocking Wizard Module

The `clk_wiz_0` module is used to convert the external  $100MHz$  clock to  $10MHz$ .

## Light Sensor Module

The `LightSensor` module contains everything needed to interact with and read values from the `ADC081S021` light sensor, including an SPI interface and slow clock generation.

## Seven Segment Display Module

The `SevenSegmentDisplay` module takes an input of 4, 4-bit hex values and displays them on the Basys 3's seven segment display. It does this by displaying one number at a time and cycling through all digits hundreds of times per second to create a full 4-digit to the human eye.

# Implementation

## Utilization Report

Name	Slice LUTs (20800)	Slice Registers (41600)	Bonded IOB (106)	BUFGCTRL (32)	MMCME2_ADV (5)
Top	65	65	17	3	1
Clocking Wizard	0	0	0	2	1
Light Sensor	43	47	0	0	0
Seven Segment Display	22	18	0	0	0

- Light Sensor:
  - The LUT is expected to be higher than Seven Segment Display because it is a much more complex module.
  - The register usage may seem initially high because there is only 41 bits of declared registers, however, it makes sense because some registers are required for storing `read_val` and the shifting operation into `read_temp_val`.
- Seven Segment Display:
  - The LUT usage is expected. Mostly because the segment decoding (4-bit to 7-bit) requires many LUTs, but also the anode decoding and slow clock creation.
  - The register usage is also expected because it is exactly equal to the amount of register bits, 2 from `currentDigit` and 16 from `slowClockCounter`.

# Timing Report

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 96.637 ns	Worst Hold Slack (WHS): -0.011 ns	Worst Pulse Width Slack (WPWS): 3.000 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): -0.023 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 3	Number of Failing Endpoints: 0
Total Number of Endpoints: 21	Total Number of Endpoints: 21	Total Number of Endpoints: 27
Timing constraints are not met.		


- The setup timing issues are caused by the Seven Segment Display's `slowClockCounter`. To solve this I would use a clock wizard (PLL or MCMM) to generate a slower clock next time.
- The hold timing issues are caused by the Light Sensor's `serialClockCounter`. To solve this I would also a clocking wizard module.

# Conclusion


This was a great lab that challenged me a lot. It forced me create test benches to test my code, which was initially a hassle, but eventually helped me iterate much quicker and get more data from my testing. I struggled to find a good way to implement a state machine, which I think this project could have done better without. I encountered many small bugs that took awhile to debug, for example `sample_trig_counter` being too small and `read_seq_ptr` being set in different `always_ff` blocks causing it to work in simulation but not synthesis. Overall, I learned that carefully writing and reading Verilog is very important and small issues can break the entire module in unexpected ways.

# Results

## In Ambient Light

 

## In No Light (Covered)

 

**In Bright Light**



